

Sequence Detector Moore Machine

Design a sequence detector implementing a Moore state machine. The state machine has one input (ain) and one output (detect). The output detect is 1 if and only if the total number of 1s received is divisible by 3

